

[Total No. of Questions - 9] [Total No. of Printed Pages - 4]  
(2123)

1366

B. Tech 3rd Semester Examination

Digital Electronics (O.S.)

EC(ID)-3001

Time : 3 Hours

Max. Marks : 100

*The candidates shall limit their answers precisely within the answer-book (40 pages) issued to them and no supplementary/continuation sheet will be issued.*

- Note :** (i) Attempt any five questions. All questions carry equal marks.  
(ii) Section E (all parts) is compulsory.  
(iii) Attempt one question from each sections A, B, C and D of the question paper.

**SECTION - A**

1. (a) Perform the following conversion:

(i)  $(1011.01)_2 \rightarrow (?)_{10}$

(ii)  $(365.24)_8 \rightarrow (?)_{10}$

(iii)  $(0.6234)_{10} \rightarrow (?)_8$

(iv)  $(2003.31)_{10} \rightarrow (?)_{16}$

(v)  $(AFB 2)_{16} \rightarrow (?)_2$  **(2×5=10)**

(b) Perform the following binary arithmetic operation.

(i)  $(10111)_2 - (11001)_2$

(ii)  $(101.11)_2 \times (111.01)_2$

1366/1400

[P.T.O.]

- (iii)  $(111110.1)_2 \div (0101)_2$
- (iv)  $(DDCC)_{16} + (BBAA)_{16}$
- (v) Subtract  $(5C)_H$  from  $(94)_H$  **(2×5=10)**
2. (a) (i) Perform  $(9)_{10} - (5)_{10}$  using 2's complement method.
- (ii) How 10's complement subtraction take place?
- (iii) Add the following BCD numbers  
0110 and 0010  
1000 0110 and 0001 0011
- (iv) Express the number  $(137)_{10}$  in BCD and binary. Explain any difference between the two results.
- (v) What do you mean by gray code? Why it is called minimum change code? **(2×5=10)**
- (b) (i) If the 7 bit Hamming code word received by a receiver is 1011011. Assuming the even parity state whether the received code word is correct or wrong. If wrong, locate the bit in error. **(5)**
- (ii) What is the need for error detection and correction code? List the various methods for the same. **(5)**

### SECTION - B

3. (a) (i) Simplify the following expression.  

$$y = \overline{(\overline{AB} + \overline{A} + AB)}$$

$$y = \overline{A\overline{B}C} + \overline{\overline{A}BC} + \overline{ABC}$$
 **(5)**
- (ii) Realize the following Boolean expression using only NAND and NOR gates.  

$$y = (AB + BC)C$$
 **(5)**

- (b) Simplify and minimise the following four variable switching function using the seine MC clusky tabulation method  
 $F(A, B, C, D) = \Sigma(0, 1, 2, 3, 4, 6, 8, 9, 10, 11)$  (10)
4. (a) (i) Simplify the following equation using the Karnaugh mapping procedure.  

$$X = \overline{A}\overline{B}\overline{C} + A\overline{C}\overline{D} + A\overline{B} + ABC\overline{D} + \overline{A}\overline{B}C$$
 (5)
- (ii) What are the limits on the fan out of a gate? Write expression for fan out. (5)
- (b) With the help of a suitable sketch describe the working of a full adder. Realise full adder using NAND gate. (10)

#### SECTION - C

5. What does the term logic family signify?
- (a) Explain (i) Resistor transistor logic (RTL)  
(ii) Emitter coupled logic (ECL) (10)
- (b) (i) What precaution are necessary for handling MOS devices? (5)
- (ii) Briefly describe the advantages and disadvantages of ECL. (5)
6. (a) Give a comparison of logic families in tabular form with respect to different parameters. (10)
- (b) Explain the working of CMOS NAND and NOR gates. (10)

#### SECTION - D

7. (a) Explain the operation of J-K master slave flip flop. (10)
- (b) With a neat diagram explain the operation of 4 bit SISO (serial in serial out) register. Draw the timing diagram and give its truth table. (10)

[P.T.O.]

8. (a) Explain the term asynchronous. Describe the working of asynchronous decade counter. **(10)**
- (b) What is a multivibrator? Explain astable multivibrator using IC555. **(10)**

### SECTION - E

9. (i) Explain the difference between weighted and non weighted code. Give example of each.
- (ii) Write the truth table of EXNOR gate.
- (iii) Explain and mention the universal gate.
- (iv) What is the difference in mapping a POS expression and an SOP expression?
- (v) What is propagation delay? Which logic family has least propagation delay?
- (vi) What is race around condition in J-K flip flop?
- (vii) What is meant by term edge triggered?
- (viii) What is the MOD number of a counter signifies?
- (ix) What two principle function are performed by a shift register?
- (x) What is meant by clipping circuits? Explain. **(2×10=20)**